

ATM Vending Machine


Project Features

- ATM to deposit or withdraw money from an account.
- Display the current balance on the seven segment display
- Use switches on the board to determine what type of Rs bill you would deposit/withdraw from the account.
 - $sw[0] = 1 \text{ Rs}$
 - $sw[1] = 5 \text{ Rs}$
 - $sw[2] = 10 \text{ Rs}$
 - $sw[3] = 20 \text{ Rs}$
 - $sw[4] = 50 \text{ Rs}$
 - $sw[5] = 100 \text{ Rs}$

Project Features

- We'll use an 8-bit counter for simplicity, the max amount we can deposit into the account is 255 Rs.
- LED's indicates following:
 - LED[0] – Max. deposit amount has reached
 - LED[1] – Ensures that only one switch is selected at a time
 - LED[2] – Can't go below this amount
- Push up button is for deposit the money
- Push down button is for withdraw the money
- Centre button to reset the ATM

Block Diagram:

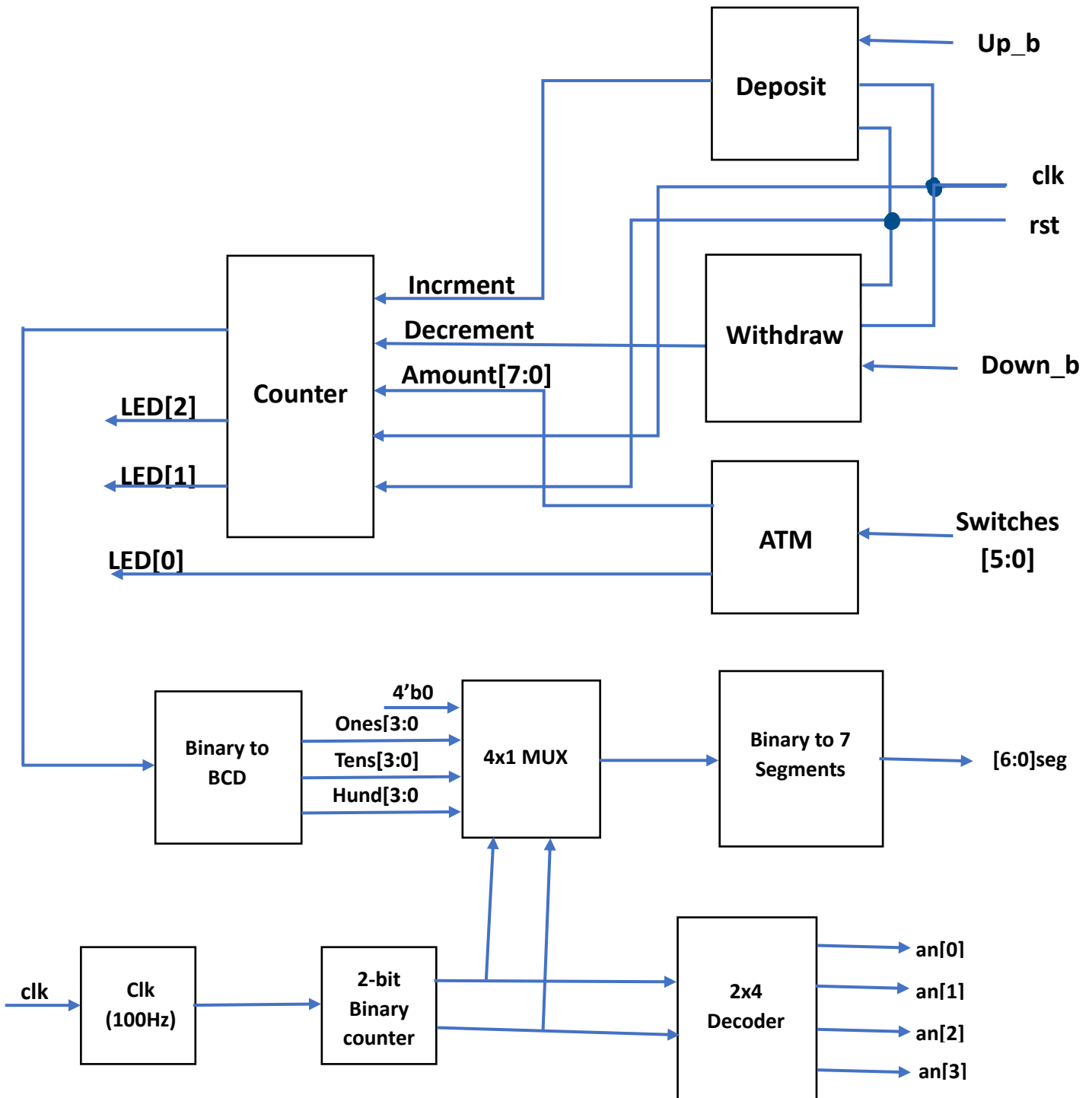

Verilog Code for ATM Vending Machine

```
module ATM_top(seg,an,dp,led,sw,push_up,push_down,rst,clk);  
    input rst,clk;  
    input push_up,push_down;  
    input [5:0] sw;  
    output dp;  
    output [2:0] led;  
    output [6:0] seg;  
    output [7:0] an;  
    assign dp = 1'b1;  
    parameter zeros = 4'b0000;  
    wire s_clk;  
    wire up_out,down_out;  
    wire inc,dec;  
    wire [1:0] sel;  
    wire [7:0] amount,count;  
    wire [3:0] mux_out,hunds,tens,ones;  
  
    user_clock M0(s_clk,clk);  
    debounce M1(up_out,push_up,clk);  
    debounce M2(down_out,push_down,clk);  
    deposit M3(inc,up_out,rst,clk);  
    withdraw M4(dec,down_out,rst,clk);  
    ATM M5(amount,led[0],sw);  
    counter M6(count,led[2],led[1],amount,inc,dec,rst,clk);  
    Binary_to_BCD_converter M7(hunds,tens,ones,count);  
    counter_2bit M8(sel,s_clk);  
    mux_4x1 M9(mux_out,zeros,hunds,tens,ones,sel);  
    Decoder M10(an,sel);  
    Binary_to_7seg M11(seg,mux_out);  
endmodule
```

RTL schematic

